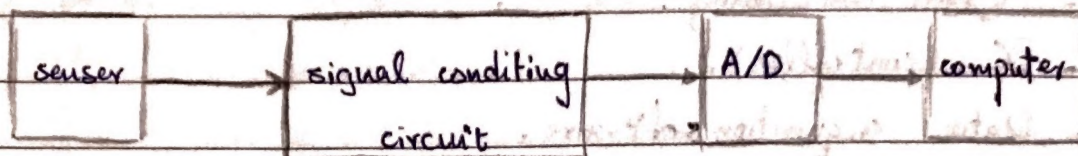


Data acquisition

تأثير الحساسات واستلام البيانات



for TTL

0 1

which means 0V 5V

from the range (0 ~ 0.8V) (2 ~ 5.5V)

for CMOS

0 1

from the range 0V 3 ~ 18V



Fundamentals of Data acquisition

- Sensor and transducer.
- Field wiring.
- Signal conditioning.
- PC (controller).
- Data acquisition software.


المجالس :

"Range" المدى

"Span" النطاق

"transfer function" scale factor : "Sensitivity" الحساسية

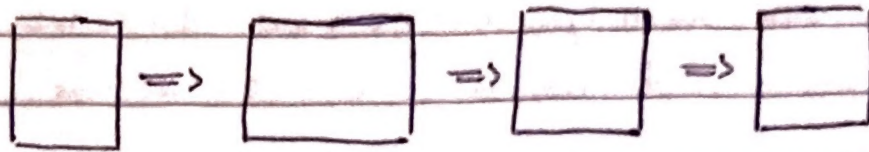* Text book : Process control instrumentation Technology
by : Curtis D. Johnson



sensor

signal
conditioning


A/D

computer

For good design

choose available Power supply (1.5, 4.5, 9, 6, 12) V.

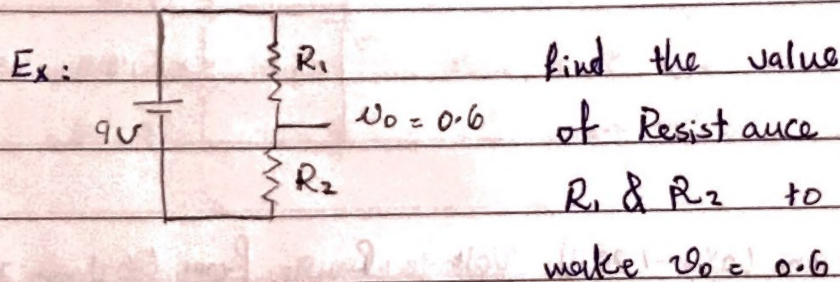choose available Resistance with suitable Power (w).



دو ديود
 (10 ~ 20) mA

from the voltage divider rule $V_0 = V_s \frac{R_2}{R_1 + R_2}$

$$0.6 = 9 \cdot \frac{R_2}{R_1 + R_2}$$

$$0.6 R_1 = (9 - 0.6) R_2 \Rightarrow R_1 = 14 R_2$$

Note range of the bridge is not fixed. It depends on the range of the voltage of the OHM.




Ex: RTD with sensitivity $1.5 \Omega/^\circ\text{C}$ and its value at $0^\circ\text{C} = 140 \Omega$, find the range ($0 \sim 80^\circ$) in ohm, design circuit to convert the range to volt


Sol:

the range From 140Ω to $(140 + 1.5 \times 80) \Omega$

Wheatstone Bridge

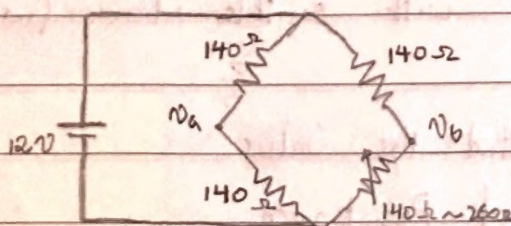

Voltage divider

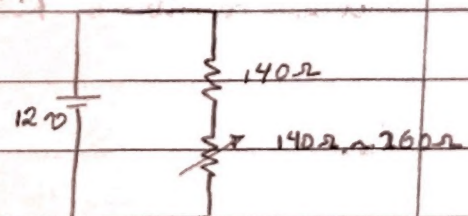

Voltage Range From ($0\text{V} \sim 1.8\text{V}$)

Voltage Range From ($6\text{V} \sim 7.8\text{V}$)

$$\Delta V = V_a - V_b ; V_a = 6\text{V}$$

$$\text{at RTD} = 140 \Omega ; V_b = 6\text{V}$$

$$\Delta V = 0\text{V}$$

$$\text{at RTD} = 260 \Omega ; V_b = 7.8\text{V}$$

$$\Delta V = 1.8\text{V}$$

Nulling equation $R_1 R_4 = R_2 R_3$




Ex: using the resistance $130\ \Omega$, $270\ \Omega$ using the RTD with sensitivity $1.5\ \Omega/^{\circ}\text{C}$ it's value at $0^{\circ}\text{C} = 140\ \Omega$, design circuit to convert the range in voltage.

Sol

use $130\ \Omega$ for R_1 & $270\ \Omega$ for R_2 and RTD for R_4 from the nulling equation

$$R_3 = \frac{R_1 R_4}{R_2} \quad ; \quad \text{where } R_4 \text{ at minimum}$$

$$R_3 = 67.4074\ \Omega$$

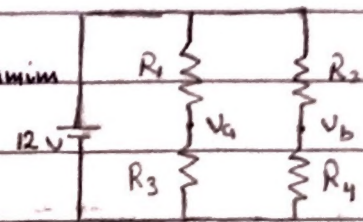

at $R_4 = 140\ \Omega$; $V_a = 4.09\ \text{volt}$, $V_b = 4.09\ \text{V}$ $\Delta V = 0\ \text{V}$

at $R_4 = 260\ \Omega$; $V_a = 4.09\ \text{V}$, $V_b = 5.88\ \text{V}$ $\Delta V = 1.79\ \text{V}$

the Range in Voltage ($0 \sim 1.79\ \text{V}$)

Ex: Pressure sensor sensitivity $0.09\ \text{V}/\text{bar}$ and its value at $0\ \text{bar} = -0.2\ \text{V}$, Determine its output range for the Pressure ($0 \sim 140\ \text{bar}$), Design signal conditioning circuit for A/D circuit reference ($0 \sim 5\ \text{V}$)

Sol :

12.4

the output range in volt from $-0.2\ \text{V}$ to $(-0.2 + 140 \times 0.09)\ \text{V}$
 لإيجاد المدى المرجعي لـ A/D

$$0 = -0.2\ \text{V} + \text{offset}$$

$$5 = 12.4\ \text{V} + \text{offset} \quad ; \quad M = 0.3968, \quad \text{offset} = 0.07436$$



$$v_0 = 0.3968 \quad v_1 + 0.07936$$

نقوم بالتحقق عن طريق الجدول التالي


v_i -0.2 6.1 12.4

v_{out} 0 2.5 5 \Rightarrow should be result

0 2.499 4.999 \Rightarrow the number from the equation

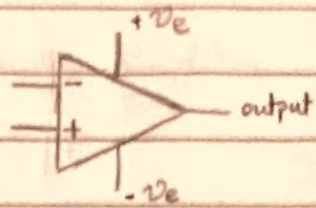
اختبرنا 6.1 لأنها في المتوسط بين -0.2 و 12.4





± 15 it's means that
the different between
the inputs can be up to
30 volt

inverting amplifier

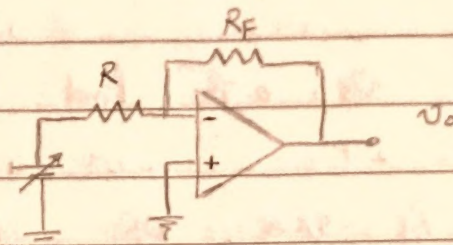

مكسب أو كسب
بالعربي gain

$$\frac{V_o}{V_i} = - \frac{R_f}{R}$$

Ex: if signals $V_s = 0.8\text{V}$, find (3%, $\frac{5}{2}$, 2.5%)

1. $R_f = 3R$

$$V_o = -3 * 0.8 = -2.4$$

let $R_i = 1\text{k}\Omega$

$$R_f = 3\text{k}\Omega$$

2. $R_f = \frac{1}{2} R_i$

$$V_o = -\frac{1}{2} * 0.8 = -0.4$$

let $R_i = 1\text{k}\Omega$

$$R_f = 500\Omega$$

3. $R_f = 2.5 R_i$

$$V_o = -2.5 * 0.8 = -2$$


let $R_i = 1\text{k}\Omega$

$$R_f = 2.5\text{k}\Omega$$

لنأخذ من ال gain العنصر في amplifier آخر لا يأخذ العنصر



non-inverting amplifier

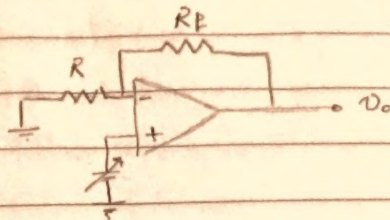

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R}$$

Ex: if signals $V_s = 0.75$ find V_o


$$R_1 = 1k\Omega \text{ so } R_f = 4k\Omega \quad \text{OR} \quad R_1 = 3k\Omega \text{ so } R_f = 12k\Omega$$

$$V_o = (1 + 4) V_s = 3.75 \text{ volt}$$

حيث وجود ال +1 في القانون



Summing Amplifier

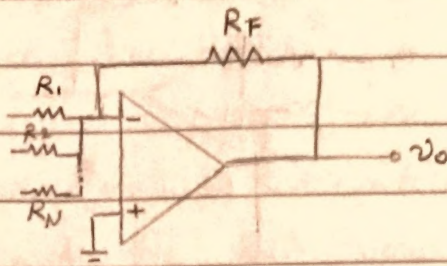

$$V_O = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \dots + \frac{R_F}{R_N} V_N \right)$$

Ex: $V_1 = 1.25$ volt, $V_2 = 0.67$ volt, $V_3 = 0.8$ volt

Find $V_1 + V_2$, $V_1 + 2V_2$, $\frac{1}{2}V_1 + 2V_2 + 0.2V_3$, The average of them

1

$$R_1 = 1k\Omega$$

$$R_2 = 1k\Omega$$

$$R_F = 1k\Omega$$

$$V_O = \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2$$

$$V_O = 1.72 \text{ volt}$$

2

$$R_1 = 1k\Omega$$

$$R_2 = 500\Omega$$

$$R_F = 1k\Omega$$

$$V_O = \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2$$

$$V_O = 1.585 \text{ volt}$$

3

$$R_1 = 500\Omega$$

$$R_2 = 2k\Omega$$

$$R_3 = 5k\Omega$$

$$R_F = 1k\Omega$$

$$V_O = \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3$$


$$V_O = 2.125 \text{ volt}$$

to find the average make the gain $\frac{1}{N}$
 N : number of them

Note: to find $V_1 - V_2$ without mines make $V_2 - V_1$



subtractor amplifier


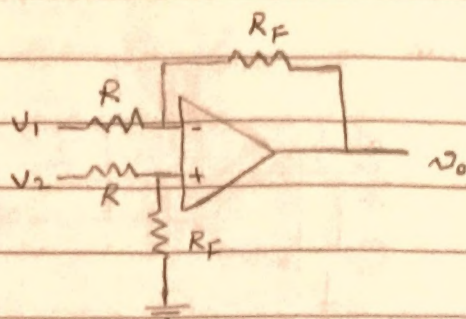


$$V_0 = -\frac{R_F}{R} (V_1 - V_2) = \frac{R_F}{R} (V_2 - V_1)$$


Ex : if $V_1 = 1.25$ volt, $V_2 = 0.87$ volt find $V_1 - V_2$,

$$V_2 - V_1$$

make $R_F = R$ to find $V_1 - V_2$

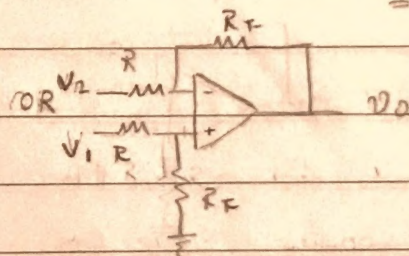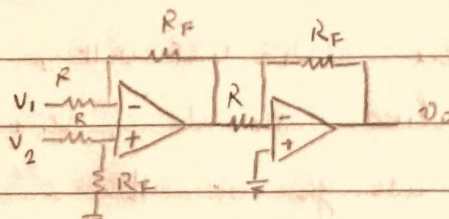


to find $V_2 - V_1$

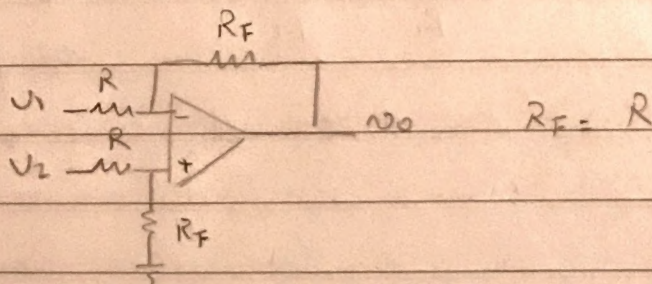

Buffer

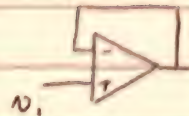we use it to split between the stages
and make more fan out



Ex: using RTD with sensitivity $1.5 \Omega/^{\circ}\text{C}$ in the temperature range ($20^{\circ} \sim 80^{\circ}$) and the RTD value at $0^{\circ}\text{C} = 120 \Omega$, calculate its range in ohm & volt.

- Design circuit to convert the range into volt (using the Bridge)
- Design signal conditioning circuit to use (0~5) ADC

Solution:

$$\text{at minimum } 20^{\circ} \quad \text{RTD} = 120 + 1.5 \times 20 = 150 \Omega$$

$$\text{at maximum } 80^{\circ} \quad \text{RTD} = 120 + 1.5 \times 80 = 240 \Omega$$

$$\text{so let } R_1, R_2, R_3 = 150$$

and the power supply 9V



$$V_a = 9 \times \frac{150}{300} = 4.5 \text{ volt}$$

$$\text{at nulling } V_b = 9 \times \frac{150}{300} = 4.5 \text{ volt}$$

$$\Delta V = 0 \text{ volt}$$

$$\text{at maximum } V_b = 9 \times \frac{240}{250 + 240} = 5.53846 \text{ volt}$$

$$\Delta V = -1.03846$$

Range in ohm ($150 \sim 240$) Ω

Range in volt ($0 \sim 1.038$) volt



to find the signal conditioning circuit

$$0 = M \cdot 0 + \text{offset}$$

$$5 = M \cdot 1.038 + \text{offset}$$

$$M = 4.81695$$

$$\text{offset} = 0$$

V_{in}	0	0.5016	1.038	inter-all V_{in}
----------	---	--------	-------	--------------------


V_{out}	0	2.5	5	\Rightarrow should be
-----------	---	-----	---	-------------------------

V_{out}	0.004m	2.416	5.002	result
-----------	--------	-------	-------	--------

from Computer Lab

using RTD: 187.635 for $\Delta V = 0.5016$

$$V_o = 4.816(V_b - V_a)$$

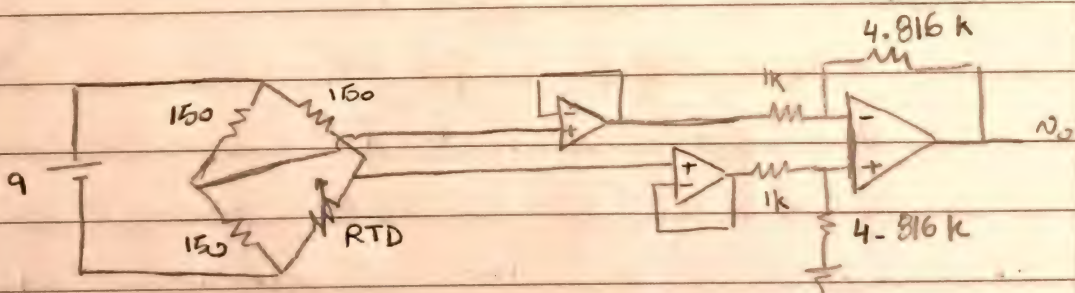

$$V_o = -\frac{R_F}{R} (V_a - V_b)$$

$$V_o = -\frac{4.816}{1} (V_a - V_b) = 4.816(V_b - V_a)$$



Ex: using RTD with sensitivity $0.39 \Omega / ^\circ\text{C}$ in the range $(0^\circ \sim 100^\circ)$, RTD = 170Ω at 0°C , use 9V supply, the two resistance 140Ω & 180Ω (using bridge)


- Calculate the range in ohm & volt
- Design signal conditioning circuit to $(0 \sim 4\text{V})$ reference ADC

Solution:

at minimum RTD = 170

at maximum RTD = $170 + 0.39 \times 100 = 209$

Range in ohm $(170 \sim 209) \Omega$

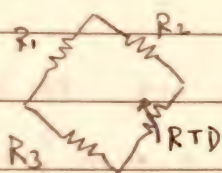

let $R_1 = 140$, $R_2 = 180 \Omega$, RTD = 170

$$\text{So } R_3 = \frac{R_1 R_2}{R_2} = 132.22 \Omega$$

$$V_a = 9 \times \frac{R_3}{R_1 + R_3} = 4.371 \text{ V}$$

$$\text{at minimum } V_b = 9 \times \frac{170}{170 + R_2} = 4.371 \text{ V}, \Delta V = 0 \text{ volt}$$

$$\text{at maximum } V_b = 9 \times \frac{209}{209 + R_2} = 4.835 \text{ V}, \Delta V = 0.464 \text{ V}$$

Range in Volt $(0 \sim 0.464) \text{ volt}$




for the signal conditioning circuit

$$0 = M \cdot 0 + \text{offset}$$

$$4 = M \cdot 0.464 + \text{offset}$$

$$M = 8.6202, \text{ offset} = 0$$

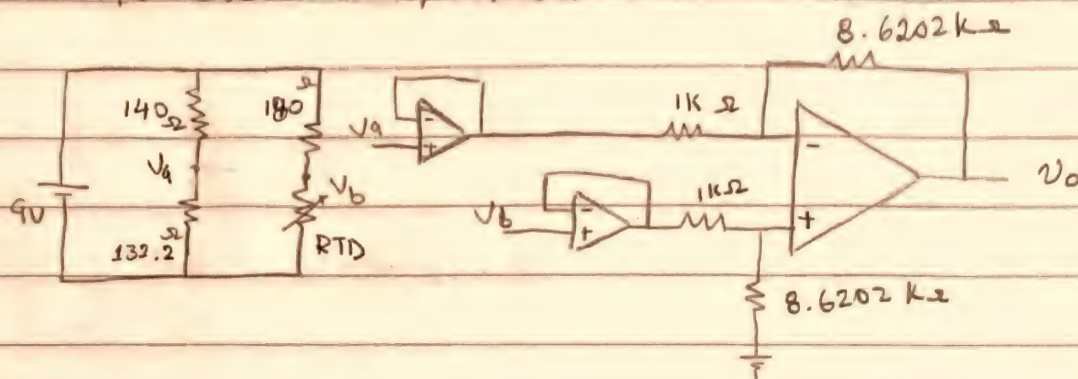

$$V_O = 8.6202 (V_B - V_A)$$

Ex: Pressure Sensor sensitivity 0.2 V/bar and its output at 0 bar = 0.8 V, calculate its range in volt (in ± 10 bar)

- Design S.C. circuit for (0~3) voltage reference ADC

Solution :

$$\text{at minimum sensor value } 0.8 + 0.2 \cdot -10 = -1.2 \text{ Volt}$$

$$\text{at maximum sensor value } 0.8 + 0.2 \cdot 10 = 2.8 \text{ Volt}$$

Range in volt (-1.2 ~ 2.8) volt

for the S.C circuit

$$0 = M \cdot -1.2 + \text{offset}$$

$$M = 0.75$$

$$3 = M \cdot 2.8 + \text{offset}$$

$$\text{offset} = 0.9$$




ملاحظات:

- * عندما تكون بداية المدخل سالبة نوعه لا offset موجب
- "بالإضافة إلى أنه نتيجة ال offset تكون موجبة"
- * عندما تكون بداية المدخل موجبة، و أكبر من صفر نوعه
- لا offset سالبا " كما أنه نتيجة ال offset تكون سالبة "
- * في حالة " $V_o = M V_i + \text{offset}$ " نستخدم Summing Amplifier
- * في حالة " $V_o = M V_i - \text{offset}$ " نستخدم Subtractor Amplifier
- و نوجد ال offset من inverting terminal

Con. Solution:

$$V_o = 0.75 V_i + 0.9$$

using Summing Amplifier

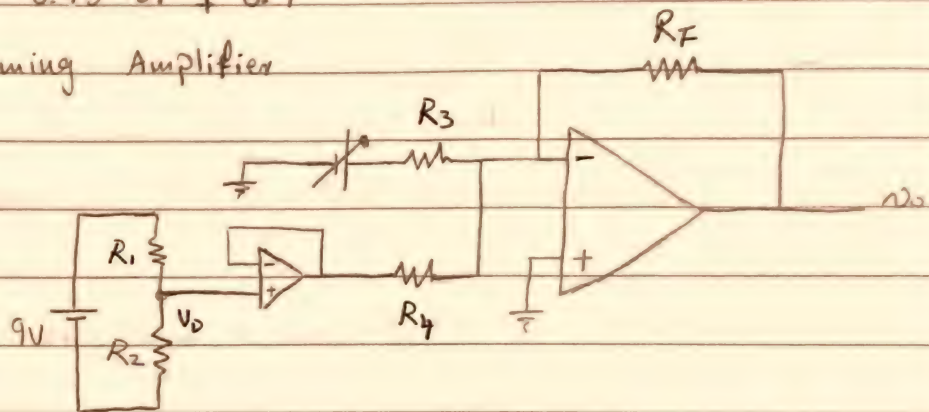

0.9

$$V_0 = 9 \times \frac{R_2}{R_1 + R_2} \Rightarrow R_1 = 9R_2$$

$$R_4 = 0.75 \text{ k}\Omega, \quad R_3 = 1 \text{ k}\Omega, \quad R_F = 0.75 \text{ k}\Omega, \quad R_1 = 9 \text{ k}\Omega, \quad R_2 = 1 \text{ k}\Omega$$

العلاقة بين $\frac{R_F}{R_3}$ يجب أن تساوي M، $\frac{R_F}{R_4}$ تساوي 1 حتى يدخل ال offset كما هو

نتوصل على ال offset عن طريق مجزأ الجهد

* يجب استخدام Buffer للفصل بين مجزأ الجهد و amplifier



Ex: Pressure sensor sensitivity 0.31 V/bar and its output at $0 \text{ bar} = -0.5 \text{ V}$.

calculate its output in the range $(\pm 12 \text{ bar})$.

Design S.C. ckt for $(0 \sim 6)$ ADC voltage reference.

Solution:

$$\text{minimum sensor Output value} = -0.5 + 0.31 * 12 = -4.22 \text{ V}$$

$$\text{maximum sensor Output value} = -0.5 + 0.31 * 12 = 3.22 \text{ V}$$

$$\text{Output range } (-4.22 \sim 3.22) \text{ V}$$


for S.C. ckt

$$0 = M * -4.22 + \text{offset}$$

$$6 = M * 3.22 + \text{offset}$$

$$M = 0.80645 \quad \text{offset} = 3.403$$

$$V_o = 0.8064 V_i + 3.403$$

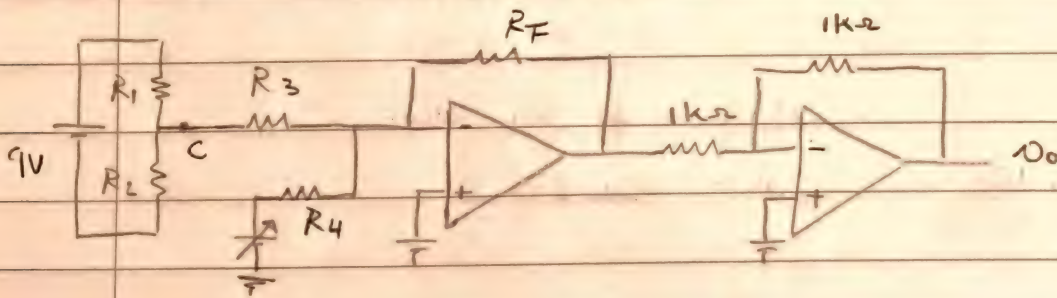

$$\frac{R_F}{R_4} = 0.8064 \quad R_F = 1 \text{ k}\Omega \quad R_4 = 1.24 \text{ k}\Omega$$

$$\frac{R_F}{R_3} = 1 \quad R_3 = 1 \text{ k}\Omega \quad \text{at point C} = 3.403 \text{ V}$$

$$\text{So } R_1 = 1.6447 R_2 \quad R_1 = 1.64 \text{ k}\Omega \quad R_2 = 1 \text{ k}\Omega$$

using voltage divider

Rule



Ex: Pressure Sensor sensitivity 0.22 V/bar and it's output at 0 bar = 0.7 V

- calculate it output in the range (0 ~ 20) bar
- Design S.C. ckt for (0 ~ 6) ADC

Solution:

minimum at 0 bar

Output Range (0.7 ~ 0.7 + 0.22 * 20)

5.1 → maximum at 20 bar

For S.C. ckt



$$0 = M * 0.7 + \text{offset}$$

$$6 = M * 5.1 + \text{offset}$$

$$M = 1.3636, \text{ offset} = -0.9545$$

$$V_o = 1.3636 V_i - 0.9545$$

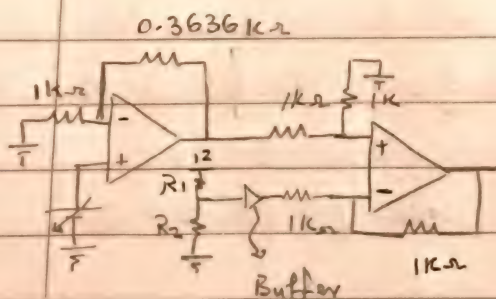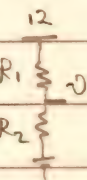for the value of offset we can take it by the voltage divider Rule with supply 12 volt $R_1 = 11.572 R_2$



هناك ثلاثة طرق للحل


1- من الطريقة الأولى نبدأ على الحصول على gain الذي يجب أن يساوي M على non-inverting amplifier

2- يجب مراعاة أن تكون non-inverting amplifier و subtractor amplifier


لذا نبدأ بمرحلة واحدة M للحصول على gain المطلوب
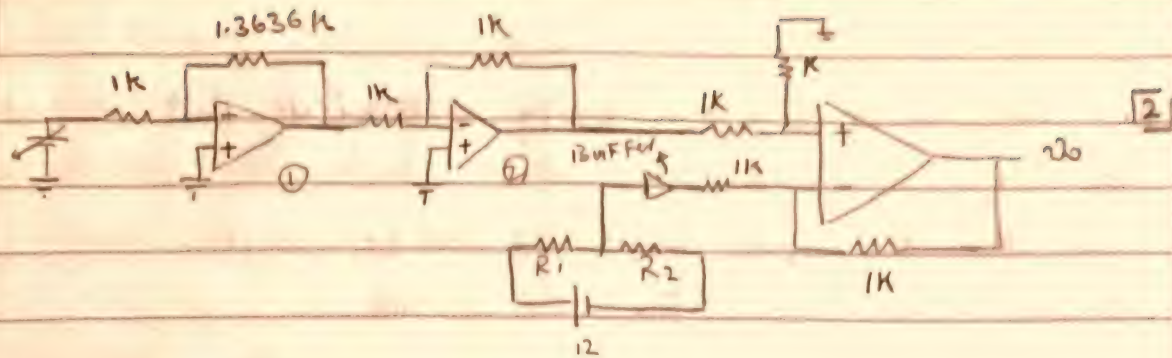
$$V_o = \left(\frac{0.3636}{1} + 1 \right) V_{in}$$





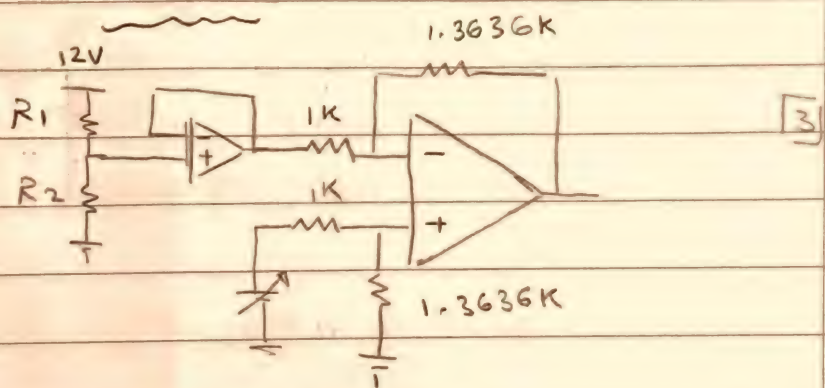في هذه الطريقة نستخدم inverting amplifier للحصول على gain $v_o = -\frac{R_F}{R} v_i$ لكن علينا مراعاة الإشارة السالبة لذا لنحصل منها نقوم بالضرب في gain أخرى بقيمة -1 وهو ما نحصل عليه من second amplifier أو subtracter amplifier



في هذه الحالة نقوم باستغلال فكرة subtracter amplifier ونقوم بتغيير قيمة ال offset لها يتناسب مع المعادلة

$$v_o = 1.3636 (v_i - 0.6999) - 0.9545 = 1.3636 v_i - 0.9545$$

حيث ندخل ال offset بالقيمة 0.6999 وإزالة عن طريق تعديل المقاومة لتصبح $R_1 = 16.145 R_2$

$$v_o = \frac{R_F}{R} (v_2 - v_1) \text{ حيث}$$

ملحوظة هامة: كلما كانت الطريقة تعتمد على amplifiers أقل كلما كانت أفضل ، لذا فالطريقة الثالثة هي الأفضل




Ex: Accelerometer sensitivity 0.2 mA/g , calculate it's output range in $(\pm 10 \text{ g})$

- Design signal conditioning circuit for $(0 \sim 3) \text{ ADC}$


Solution:

Output Range in Amp $(0.2 \text{ mA} \cdot 10 \sim 0.2 \text{ mA} \cdot 10) \text{ Amp}$

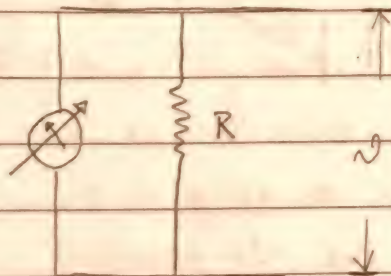to convert current to voltage there is two ways



$$V = R \cdot I$$

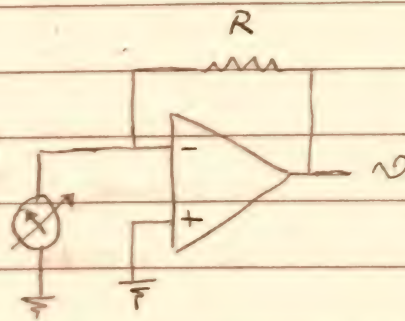

$$V = -RI$$

في كلا الحالتين يجب مراعاة قيمة المقاومة لا تها سطح
Voltage Range

in case we choose $1 \text{ k}\Omega$

the Output Range in Volt
 $(-2 \text{ V} \sim 2 \text{ V})$

For example

$$100 \text{ k}\Omega \Rightarrow \pm 200 \text{ V}$$

$$10 \text{ k}\Omega \Rightarrow \pm 20 \text{ V}$$



for S.C. act



$$0 = M \cdot 2 + \text{offset}$$

$$3 = M \cdot 2 + \text{offset}$$

$$M = 0.75, \text{ offset} = 1.5$$

$$V_o = 0.75 V_i + 1.5$$

to remove
the negative
sign

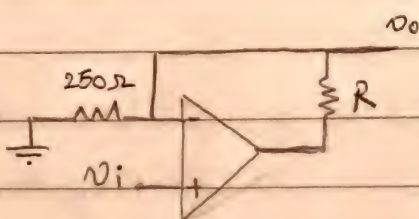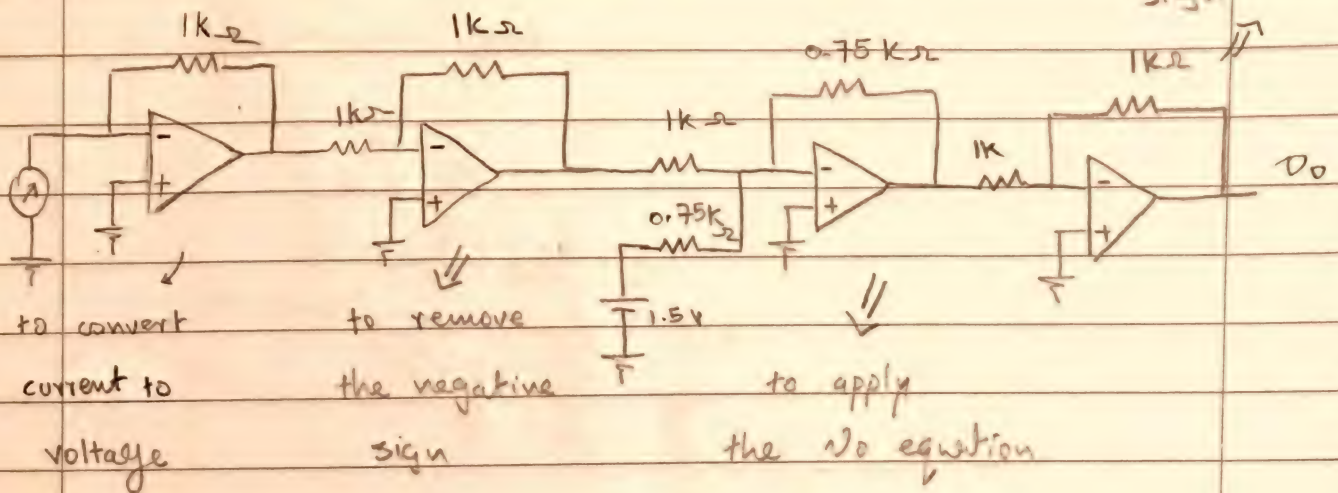

4mA ~ 20mA transmitter

has current range 4mA ~ 20mA

Voltage range (1 ~ 5)V

* مدى التيار يبدأ من 4mA حتى نفوق بينه المجهس إذا كان
مطلوب أو لا حيث أن 0mA تعني أن المجهس مطلوب و 4mA
تعني أن المجهس يقد


* يجب اختيار قيمة مقاومة صغيرة حتى لا يكون بشكل صحيح



Ex: Accelerometer sensitivity 0.1 V/g for the range $(0 \sim 8) \text{ g}$
 we want to send Accelerometer data for 20 m to
 use it for $(0 \sim 5) \text{ ADC}$

Solution:

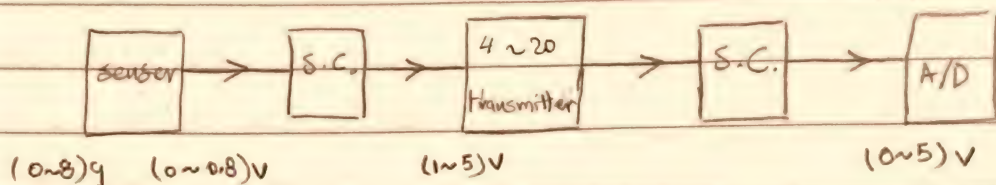Output range of the Accelerometer $(0.1 \cdot 0 \sim 0.1 \cdot 8) \text{ V}$



لأن T.cct يقبل المدى من 1V إلى 5V و A/D يحتاج المدى من 0V إلى 5V
 منجب للاستقبال S.C. الأولى لتضيق خرج المرسـ
 ل T.cct والآخرى لتضيق المتأخر لتحويل A/D

بالنسبة لـ First S.C. سنقوم بزيادة 1 فقط ليصبح
 المدى من 1V إلى 1.8V وهذا المدى يقبل به في T.cct

بالنسبة لـ second S.C. سنقوم باتباع الخطوات المعتادة


$$0 = M \cdot 1 + \text{offset}$$

$$5 = M \cdot 1.8 + \text{offset}$$

$$M = 6.25, \text{ offset} = -6.25$$

$$V_0 = 6.25 \cdot 1.2 - 6.25$$



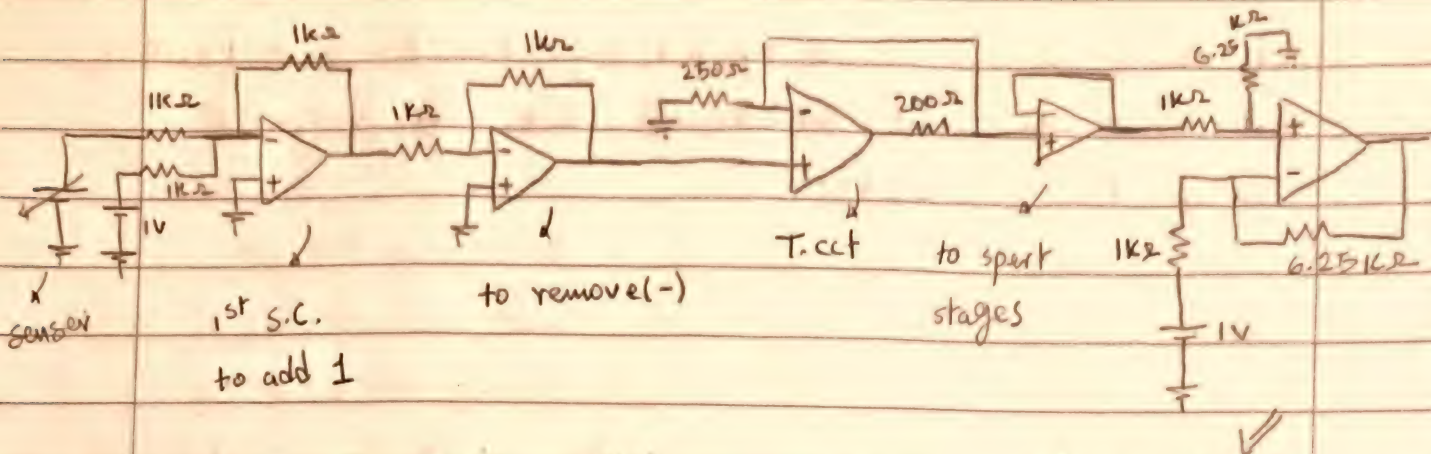

$$V_o = 6.25 (V_i - 1)$$



Ex: Temperature sensor sensitivity $0.2 \text{ mV}/^\circ\text{C}$ in the range $(0 \sim 100)^\circ\text{C}$ and its output at $0^\circ\text{C} = 12 \text{ mV}$.

- Design S.C. circuit for $(0 \sim 8)$ ADC...
- Write the temperature equation

Solution:

32 mV

Output Range $(12 \text{ mV} \sim 12 \text{ mV} + 0.2 \text{ mV} \cdot 100)$


for S.C. ckt

$$0 = M \cdot 12 \text{ m} + \text{offset}$$

$$8 = M \cdot 32 \text{ m} + \text{offset}$$

$$M = 400 \quad \text{offset} = -4.8$$
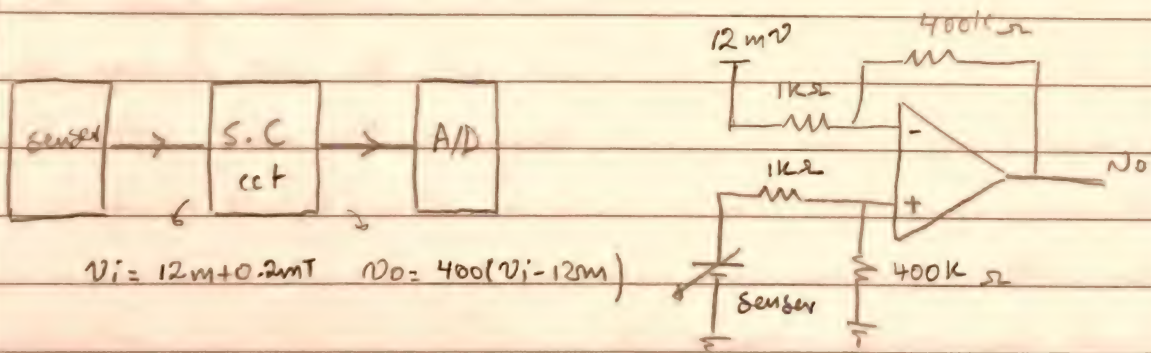
$$V_o = 400 V_i - 4.8 = 400(V_i - 12 \text{ m})$$




$$V_o = 400(12 \text{ m} + 0.2 \text{ mT} - 12 \text{ m})$$

$$V_o = 80 \text{ mT} \Rightarrow T = \frac{V_o}{80 \text{ m}}$$



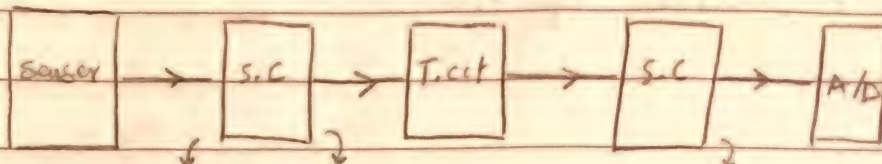Ex: For the last example in the last lecture write acceleration equation.



$$v_i = 0.1 * A \quad v = v_i + 1$$

$$v_o = 6.25 v - 6.25$$


$$v_o = 6.25 (v_i + 1) - 6.25 = 6.25 (0.1 A + 1) - 6.25$$

$$v_o = 6.25 * 0.1 A + 6.25 - 6.25$$

$$A = \frac{v_o}{0.625}$$



Comparator

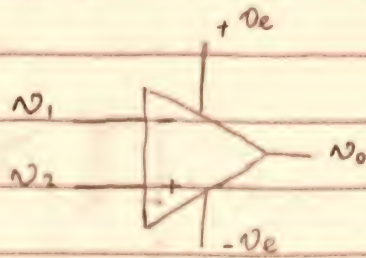

when

$$V_1 > V_2$$

$$V_0 = -15$$

LM 741 voltage supply


$$\pm 22 \text{ Volt}$$

$$\pm 18 \text{ Volt}$$

$$V_2 > V_1$$

$$V_0 = 15$$

IC 8

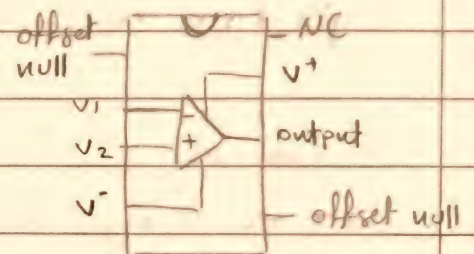

Ex: using comparator, Design circuit to operate Fan if the temperature is more than 25°C (use LM 35 sensitivity $10\text{mV}/^\circ\text{C}$)

by using potentiometer between offset null


Solution

250mV

we can get zero offset

at 25°C the output of LM35 = $10\text{mV} \times 25$

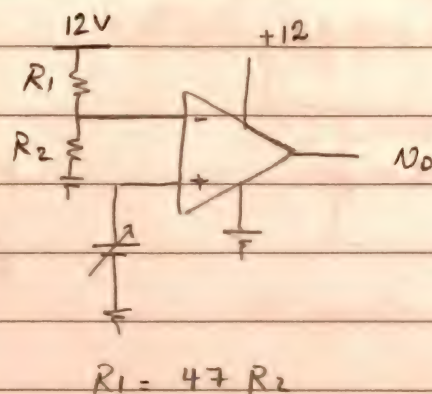قوة بتوصلها لـ Fan
inverting input
non-inverting input
خرج الحساس موجب لـ Fan
Fan




$$R_1 = 47 R_2$$



Ex: using comparator, Design circuit to operate Heater if the temperature is less than 18°C (Temp. sensor sensitivity $8\text{mV}/^{\circ}\text{C}$)

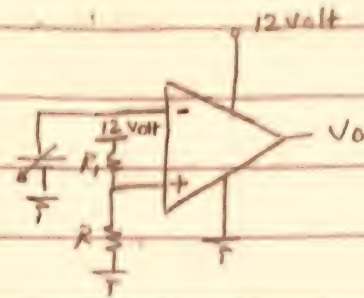Reference voltage $18 \times 8\text{m} = 144\text{mV}$



نقوم بتوصيل الحساس بالـ V_1 لأنه عند
تكون أقل من V_2 سيكون الخرج موجب
"كأن V_2 أكبر من V_1 "

$$R_1 = 82.33 R_2$$

Ex: using comparator, Design circuit to operate Heater if temperature is less than 18°C and operate fan if temperature is more than 30°C (sensor sensitivity $5\text{mV}/^{\circ}\text{C}$)

Solution

Reference voltage for $18^{\circ}\text{C} = 90\text{mV}$

Reference voltage for $30^{\circ} = 150\text{mV}$


for 18°C

$$R_1 = 132.3 R_2$$

for 30°C


$$R_3 = 79 R_4$$

to 12 voltage supply

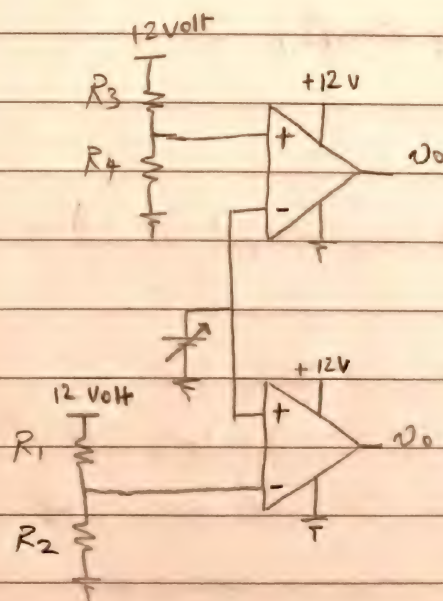


2018/4/23


12th lecture

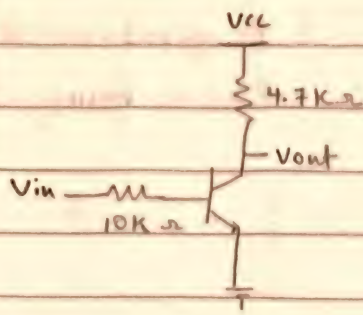


Not gate

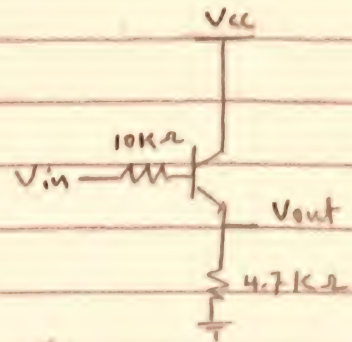


Buffer gate

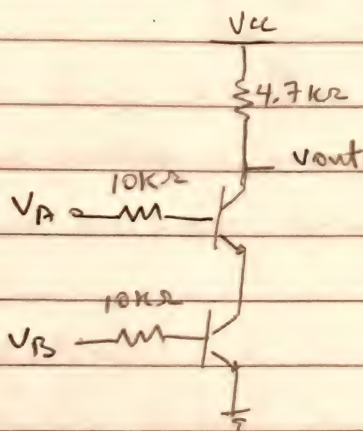


NAND gate

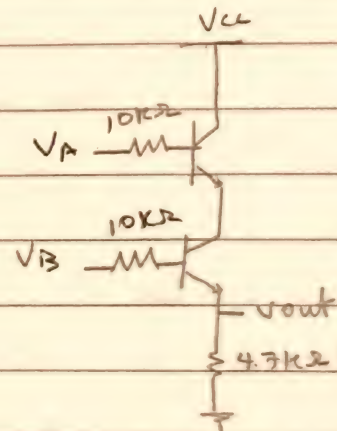

AND gate

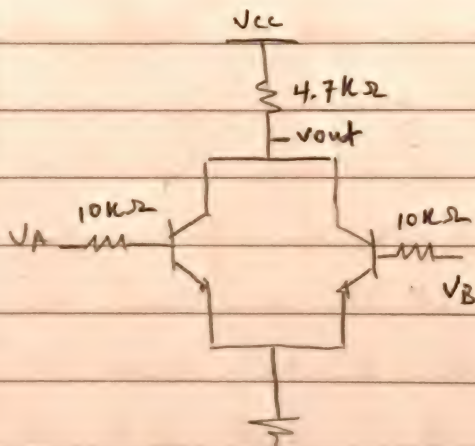


NOR gate

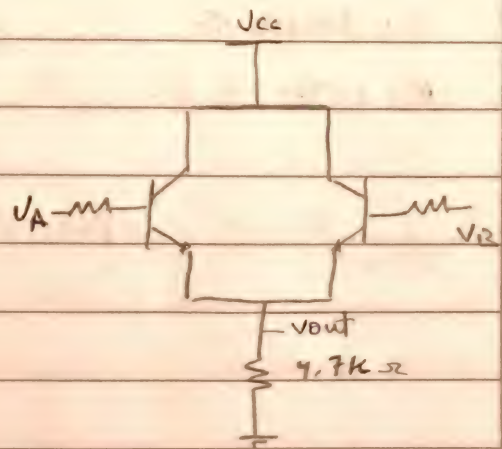

OR gate



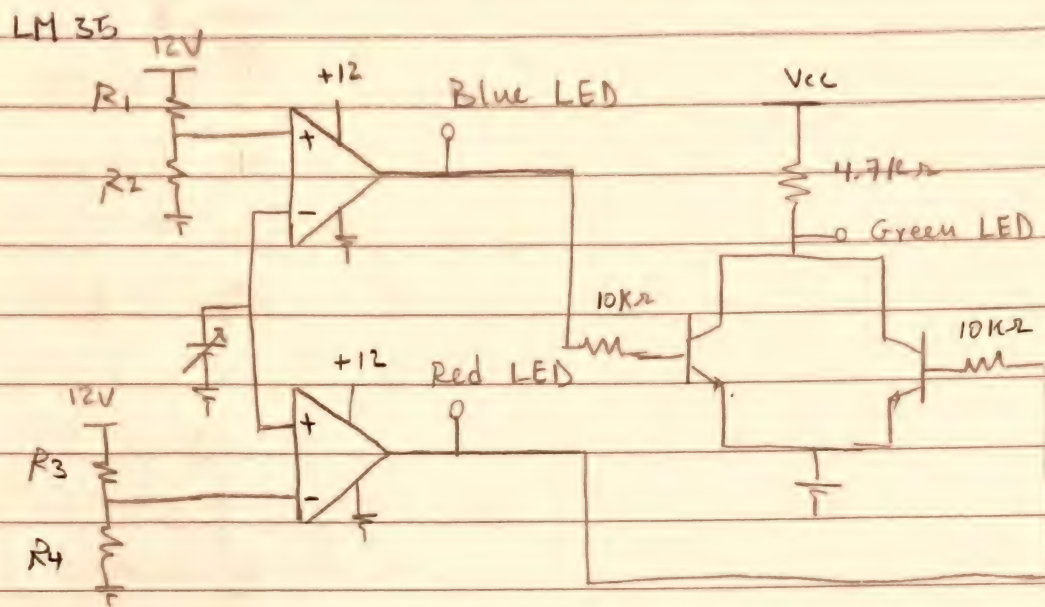Ex: Design circuit operate Red LED if Temperature is more than 37°C and operate blue ^{LED} if temperature is less than 15°C and Green LED in between using LM 35



Reference for $15^{\circ}\text{C} = 180\text{mV}$

Reference for $37^{\circ}\text{C} = 370\text{mV}$

for voltage supply 12 volt

$$R_1 = 65.67 R_2$$


$$R_3 = 31.43 R_4$$



Filters

Low Pass Filter

$$f_c = \frac{1}{2\pi RC}$$

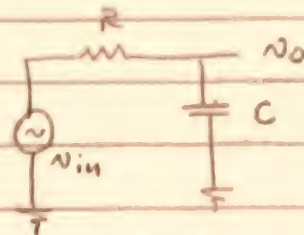

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

Ex: Design Filter to attenuate the noise to 1% and calculate the effect of the filter on the signal if the signal = 5V (1kHz) and the noise = 200mV (320kHz)

Solution

$$1\% = \frac{1}{\sqrt{1 + \left(\frac{320K}{f_c}\right)^2}} \Rightarrow f_c = 3.2 \text{ kHz}$$

the effect on the signal $\frac{1}{\sqrt{1 + \frac{1K}{3.2K}}} = 95.4\%$

assume $C = 2.2\mu F$ so $R = 22.607\Omega$ $f_c = \frac{1}{2\pi RC}$

to small so we try another value

$C = 0.1\mu F$ so $R = 497.35\Omega$ doesn't a standard value

we take 510Ω $f_c = 3.202 \text{ kHz}$


the effect on the noise become 1.00057%

* Filter make some delay



High Pass Filter
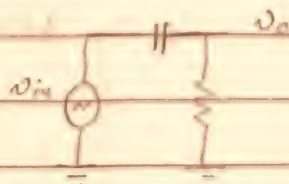
$$\frac{V_o}{V_i} = \frac{F_s/F_c}{\sqrt{1 + \left(\frac{F_s}{F_c}\right)^2}}$$



Ex: Design filter to attenuate 50Hz noise signal from the required 4 kHz signal.

Solution

If we want to attenuate the noise 1%

$$0.1\% = \frac{50/F_c}{\sqrt{1 + \left(\frac{50}{F_c}\right)^2}} \Rightarrow F_c = 4.9 \text{ kHz}$$

The attenuation on the required signal = 63.23%

this value is not good so we try another value

For 5% attenuated in the noise signal

$$5\% = \frac{50/F_c}{\sqrt{1 + \left(\frac{50}{F_c}\right)^2}} \Rightarrow F_c = 998.7 \text{ Hz}$$

The attenuation on the required signal = 93.02%




for 10% attenuate on the noise


$F_c = 492.4 \text{ MHz}$

and the attenuation on the required signal = 99%.

* Multiplexer

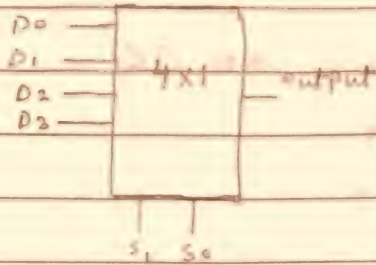

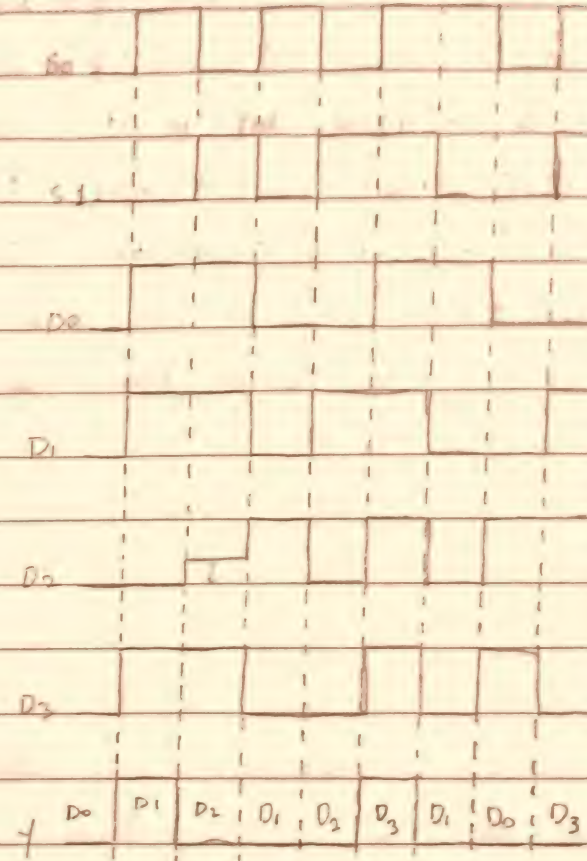ملاحظة: نحتاج ٤ مدخلات Multiplexer
١ input ، ١ output
١ selection



Digital Mux

لماذا نستخدم Multiplexer ؟

- يوفر S.C. cct. حيث أنه لو هناك أكثر من sensor من نفس النوع نقوم بتوصيلهم بال Multiplexer ، ١ output ندخله ك input لل S.C. cct.



* Analogy to Digital converter

$$V_{in} = V_m$$

$V_{re}^{+ -}$ هو المرجع الذي والمثل للإشارة

unipolar (الطاقة الموجبة) : (0 ~ 5) أو (-5 ~ 0)

Bipolar (ثنائي القطبية) : (± 2) أو (± 5)


start of conversion : SOC

Output Enable : OE

End of conversion : EOC

تتم مراقبته من قبل الفالغ مراقبة شديدة

هل هو متحول أو لا

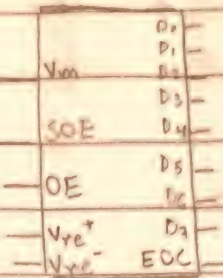

8bit ADC



* Analog to Digital converter :

Resolution (ΔV) : أقل قيمة لـ V_{in} يستطيعها المحول لزيادة بت واحد
1 bit

$$\Delta V = \frac{\text{Voltage reference}}{2^N} = \frac{V_{ref}^+ - V_{ref}^-}{2^N}$$

حيث N : عدد البتات

مثال : 4 بتات : V_{in} محوّل A/D أدق

Ex: unipolar V_{ref} (10 ~ 0) with 4-bit output.

$$\Delta V = \frac{10 - 0}{2^4} = 0.625$$

Digital Output = $\frac{\text{Analog input}}{\Delta V} \Rightarrow$ for unipolar

Ex: if input 5V, 10V with the same A/D ? what is the Digital Output.

$$\text{Digital output} = \frac{\text{Analog input}}{\Delta V} = \frac{5}{0.625} = 8 = 1000$$


Digital output = $\frac{10}{0.625} = 16$ which is not valid value
because the Maximum value is 15



Ex: What is the output of the following ADC, and what is the analog input value if digital output is $(A7)_H$

Solution:
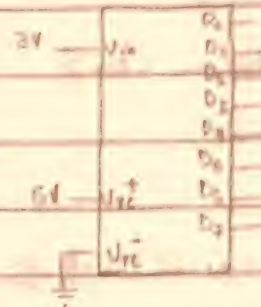
$$\Delta V = \frac{5-0}{2^8} = 19.53 \text{ mV}$$



$$\text{Digital output} = \frac{3}{19.53 \text{ mV}} = 153.8 = 153 \pm 1$$

$$(10011001)_2$$

$$\text{Digital output } (A7)_H = (167)_{10}$$

$$\text{Analog input} = \text{Digital output} \cdot \Delta V = 3.26 \text{ V}$$

Ex: temperature sensor sensitivity $0.8 \text{ mV}/^\circ\text{C}$ in the range $(0 \sim 60^\circ\text{C})$ and its output value at $0^\circ\text{C} = 0.75 \text{ V}$.

Design S.C.cct. for $(0 \sim 5) \text{ V}$ ADC and what is the temperature final equation.

Solution:


$$\text{Output sensor range } (0.75 \sim 0.75 + 0.8 \text{ m} \cdot 60)$$

$$0 = 0.75 \cdot M + \text{offset} \quad M = 104.1667$$


$$5 = 0.798 \cdot M + \text{offset} \quad \text{offset} = -78.125$$
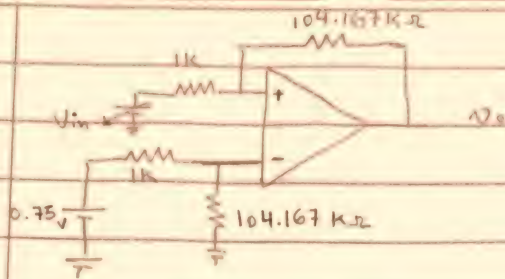
$$V_o = 104.167 V_i - 78.125 = V_o = 104.167 (V_i - 0.75)$$





Signal Conditioning circuit

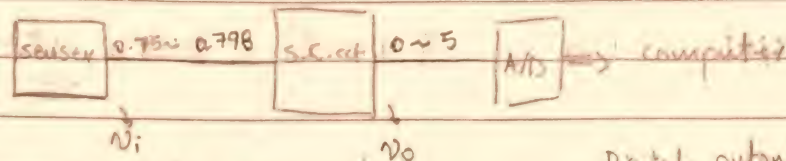

$$= (0.75 + 0.8mT)$$

$$= 104.167(V_i - 0.75)$$

$$\text{Digital output} = \frac{V_o}{\Delta V}$$

$$\text{Digital output} = \frac{V_o}{\Delta V} = \frac{104.167(V_i - 0.75)}{\Delta V} = \frac{104.167((0.75 + 0.8m * T) - 0.75)}{\Delta V}$$

$$T = \frac{\text{Digital output} * \Delta V}{0.8m * 104.167}$$



2018/5/21

16th lecture

Analog to Digital "bipolar"

$$\Delta V = \frac{V_{ref}^+ - V_{ref}^-}{2^N}$$

$$\text{Digital Output} = \frac{\text{Analog input} + V_{ref}^+}{\Delta V} = \frac{\text{Analog input} - V_{ref}^-}{\Delta V}$$

Ex: For Bipolar ADC with $V_{ref} \pm 3V$, $V_{in} 1.5V$, 8-bit output what is the Digital output

$$\Delta V = \frac{3 - (-3)}{2^8} = 23.4375 \text{ mV}$$

$$\text{Digital Output} = \frac{1.5 + 3}{23.4375 \text{ mV}} = 192 \quad (1100 \ 0000)_B$$

Ex: For Bipolar ADC with $\pm 3V$ and 8bit output what is the Digital output for the input 0V

$$\Delta V = \frac{3 - (-3)}{2^8} = 23.4375 \text{ mV}$$

$$\text{Digital Output} = \frac{0 + 3}{\Delta V} = 128 \quad (1000 \ 0000)_B$$




Ex: Using an accelerometer which sensitivity 10 mV/g in the range $\pm 20 \text{ g}$, Design S.C. ckt. For ADC which reference $\pm 5 \text{ V}$ with 8-bit output, what is the ADC output at 3 g , -7 g , what is the acceleration equation for this circuit

Solution: -200 mV 200 mV
 Sensor output range ($-20 * 10 \text{ mV} \sim 20 * 10 \text{ mV}$)

$$-5 = -200 \text{ mV} \cdot M + \text{offset} \quad M = 25$$

$$5 = 200 \text{ mV} \cdot M + \text{offset} \quad \text{offset} = 0$$

$$V_o = 25 V_i$$

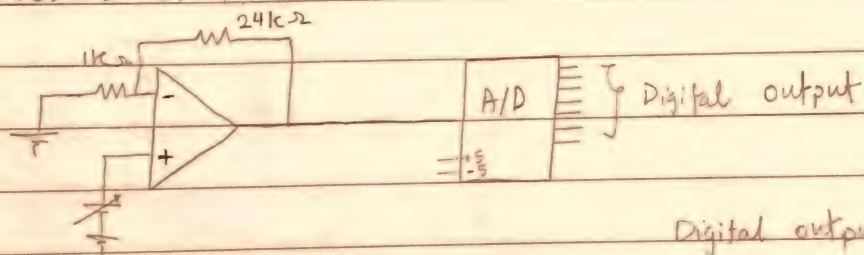


$$\text{Digital output} = \frac{\text{Analog} \cdot 5}{\Delta V}$$

$$V_o = \left(1 + \frac{R_F}{R}\right) V_i$$

$$\Delta V = \frac{5 - (-5)}{2^8} = 39.0625 \text{ mV}$$

Acceleration	3 g	-7 g
$V_i = A * 10 \text{ m}$	30 mV	-70 mV
V_o	0.75 V	-1.75 V
Digital output	$147.2 \approx 147$	$83.2 \approx 83$
	$(10010011)_2$	$(01010011)_2$



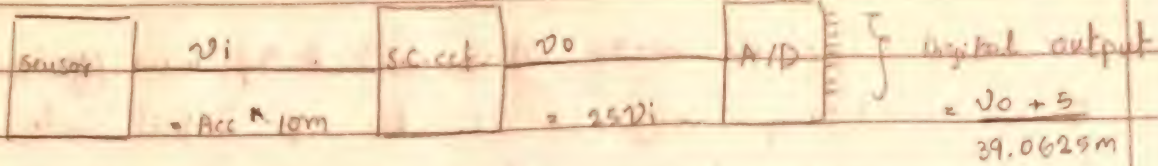

$$\text{Digital output} = \frac{V_0 + 5}{39.0625\text{m}} = \frac{25V_i + 5}{39.0625\text{m}} = \frac{25 * 10\text{m} * \text{Acc} + 5}{39.0625\text{m}}$$

$$\text{Acc} = \frac{(\text{Digital output} * 39.0625\text{m}) - 5}{25 * 10\text{m}}$$




Ex: Using barometer which sensitivity 10 mA/bar and its output at zero bar is 25 mA , Design S.C. ckt. for the range $\pm 10 \text{ bar}$ and using ADC ($V_{\text{ref}} \pm 2 \text{ V}$), what is the digital output of ADC at -2 bar , $+3.5 \text{ bar}$, what is the pressure equation will using in the program.

Solution:

$$-75 \text{ mA} \sim 125 \text{ mA}$$

$$\text{Sensor Range Output } (25 \text{ m} + -10 \times 10 \text{ m}) \sim (25 \text{ m} + 10 \times 10 \text{ m})$$

First convert current to voltage.

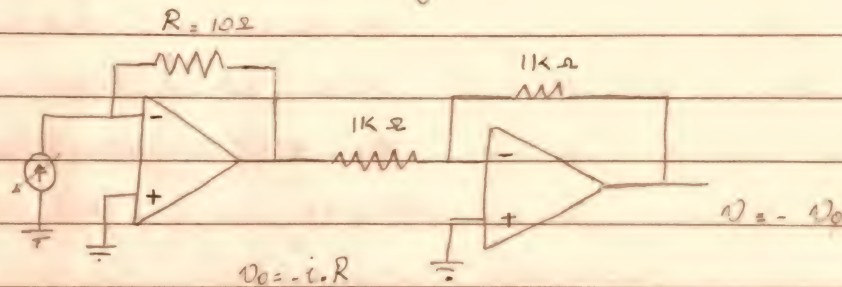

so the Output Range now will be $(-0.75 \sim 1.25) \text{ V}$

then the S.C. ckt

$$-2 = -0.75 \text{ M} + \text{offset}$$


$$\text{M} = 2$$

$$2 = 1.25 \text{ M} + \text{offset}$$

$$\text{offset} = -0.5$$

$$V_0 = 2V_i - 0.5 = 2(V_i - 0.25)$$




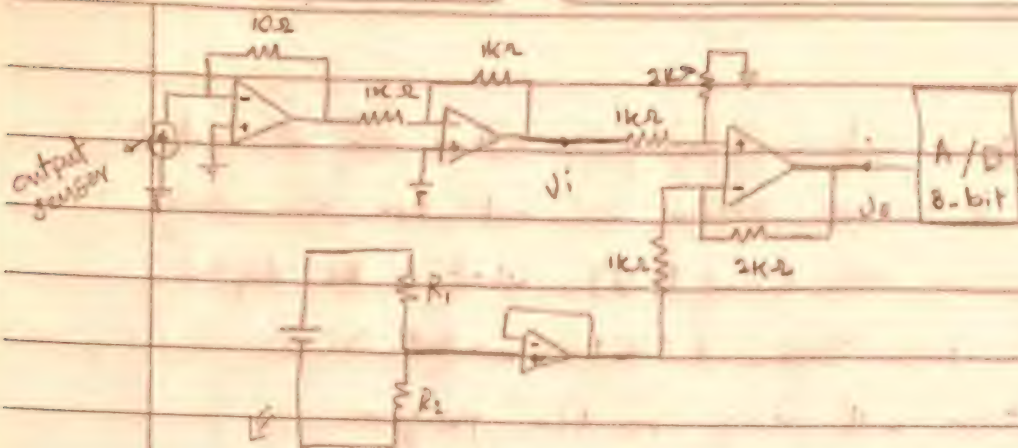

$$0.25 = \frac{3 \times R_2}{R_1 + R_2} \Rightarrow R_1 = 11 R_2$$

Pressure	-2 bar	3.5 bar
Output sensor ($25 \text{ m} + 10 \times P$)	5 mV	60 mV
V_i (0.5×10)	0.05 V	0.6 V
V_o ($2V_i - 0.5$)	-0.4	0.7
Digital output ($\frac{V_o + 2}{\Delta V}$)	$102.4 \approx 102$ (01100110) _B	$172.8 \approx 173$ (10101101) _B
$\Delta V = \frac{2 - (-2)}{2^8} = 15.625 \text{ mV}$		

Now the equation

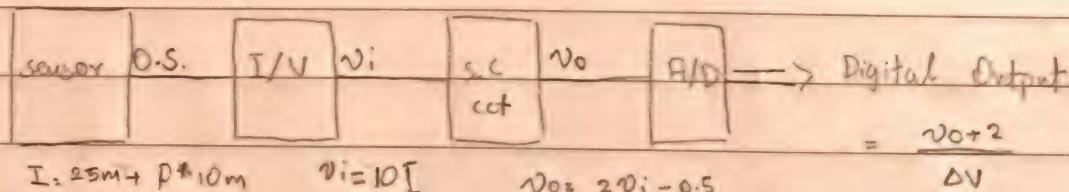


$$\begin{aligned} \text{Digital Output} &= \frac{V_o + 2}{\Delta V} = \frac{2V_i - 0.5 + 2}{\Delta V} = \frac{20I - 0.5 + 2}{\Delta V} \\ &= \frac{20 \times 25 \text{ m} + 20 \times P \times 10 \text{ m} - 0.5 + 2}{\Delta V} \end{aligned}$$

$$P = \frac{\text{Digital Output} \times \Delta V - 2}{0.2}$$



* Digital to analog (DAC)

input digital data

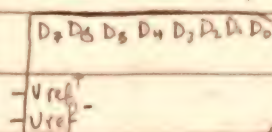

no analog output data

For unipolar

$$\Delta V = \frac{V_{ref}}{2^N} \rightarrow \text{number of input bits}$$

$$\text{analog output} = \text{Digital input} * \Delta V$$

Ex: what is the analog value of the Digital input $(01010101)_B$ with the $V_{ref} (0 \sim 4)$

 $(85)_D$

$$\Delta V = \frac{4}{2^8} = 15.625 \text{ mV}$$

$$\text{Analog value} = 85 * \Delta V = 1.328 \text{ V}$$

Ex: For the DAC with 8-bit input and $V_{ref} (0 \sim 4)$ what is the value of digital input if the analog value 2.35 V?

$$\text{Digital input} = \frac{\text{Analog Output}}{\Delta V} = \frac{2.35}{15.625} = 150.4 \approx 150 \quad (10010110)_B$$



for bipolar

$$\Delta V = \frac{V_{ref}^+ - V_{ref}^-}{2^N}$$

$$\text{Analog output} = \text{Digital input} \cdot \Delta V - V_{ref}^+$$


Ex: what is the analog value for DAC with 8-bit input and ± 3 Vref of the following 0111000, 00001100, 10100000

$$\Delta V = \frac{6}{2^8} = 23.4375 \text{ mV}$$

$$\text{Analog output} = (\Delta V \cdot \text{Digital input}) - 3$$

Binary Digital input	0111000	00001100	10100000
Decimal Digital input	120	12	160
Analog output	-0.1875	-2.71875	0.75

* Voltage to Frequency converter (VFC)

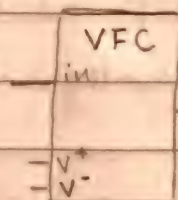


output

the output is pulses



Ex: if VFC has 1kHz/V what is the output if the input 1.25V
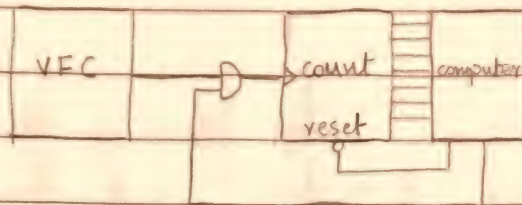
$$\text{Output} = 1.25\text{V} \times 1\text{kHz/V} = 1250\text{Hz}$$



نستعمل reset لتفجير counter لأنه تراكبي يقوم بتجميع القراءات معاً و لتجديد زمن الدورة الواحدة

Ex: if VFC has 1kHz/V with $T = 0.25$ and input 3V , what is the counter output?

$$\text{VFC output} = 3\text{V} \times 1\text{kHz/V} = 3000\text{Hz}$$

$$\text{counter output} = 3000\text{Hz} \times \frac{0.2}{1\text{Hz}} = 600$$

ملحوظة: البعض يعتقد أن هذه الدائرة هي أفضل في التحويل من Analog إلى Digital



Ex: if counter output = 150 what is the input if $T = 0.25$ and VFC has 1kHz/V

$$\text{counter input} = \frac{150}{0.2} = 750\text{Hz}$$

$$\text{VFC input} = \frac{750\text{Hz}}{1000\text{Hz/V}} = 0.75\text{V}$$



Data acquisition and conversion

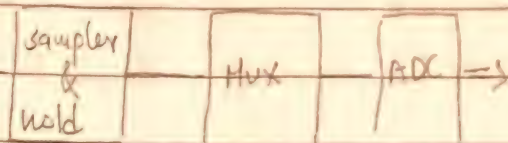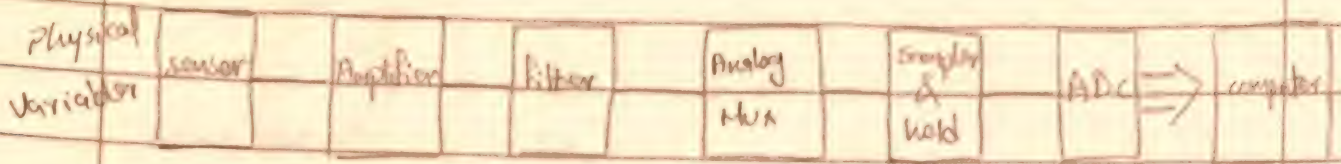


ADC conversion time: Δt_{ADC} \rightarrow Δt_{ADC} \rightarrow Δt_{ADC}

Sampler rate: f_s

↳ one of the most critical factors when selecting an board sampling rate (speed), for example 1K sample.

The sampling rate is a measure of how rapidly the ADC board can scan the input channel and identify the discrete value of signal present with respect to reference signal

cycle = Time for sampler

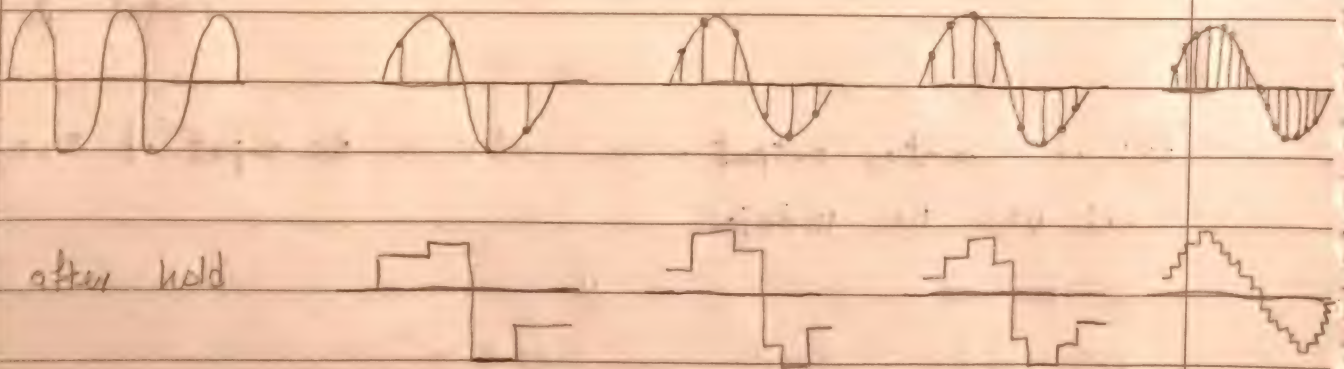

if the sampling rate is too slow, then a completely different waveform of lower frequency is constructed from the data required, this effect is called aliasing. To avoid aliasing it's necessary that the sampler rate is be at least twice of the highest expected frequency input.

Over sampling : will provide a true picture of time course of the event being studied but too much over sampling will result in very large data file.

* Sensor :

Thermal sensors

Relative temperature Scale

$$T(^{\circ}\text{C}) = T(^{\circ}\text{K}) - 273.15$$

$$T(^{\circ}\text{F}) = T(^{\circ}\text{R}) - 459.6$$

$$T(^{\circ}\text{F}) = \frac{9}{5} T(^{\circ}\text{C}) + 32$$

R: Rankine, K: kelvin, F: Fahrenheit, C: Celcius

Ex: Amatenal has temperature of 335°K Find the temperature in $^{\circ}\text{R}$

$$T(^{\circ}\text{C}) = T(^{\circ}\text{K}) - 273.15 \quad \Rightarrow \quad T(^{\circ}\text{C}) = 61.85$$

$$T(^{\circ}\text{F}) = \frac{9}{5} T(^{\circ}\text{C}) + 32 \quad \Rightarrow \quad T(^{\circ}\text{F}) = 143.33$$

$$T(^{\circ}\text{R}) = T(^{\circ}\text{F}) + 459.6 \quad \Rightarrow \quad T(^{\circ}\text{R}) = 602.93$$




2018/6/4

20 lecture

Examples:

if VFC has 5 KHz/V and the reset time of the counter 0.02 sec what is the output if

- the input 1.25 V
- the input 2.43 V

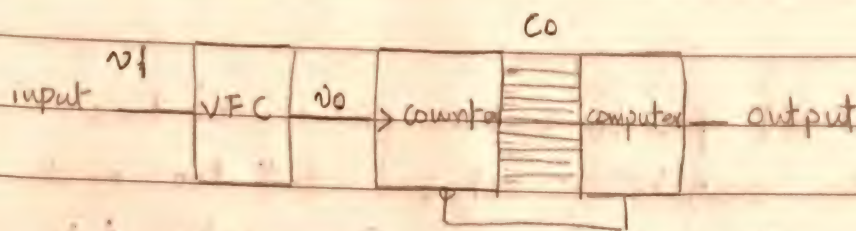

Solution

a)

$$V_o = \text{input} * 5\text{ KHz/V} = 6250\text{ Hz}$$

$$C_o = V_o * T = 125$$

$$b \quad V_o = 2.43 * 5\text{ K} = 12150\text{ Hz}$$

$$C_o = 12150 * 0.02 = 243$$

the equation of the system:

$$C_o = V_o * T = V_i * \text{rate} * T$$


$$V_i = \frac{C_o}{\text{rate} * T}$$



Temperature sensors give an output proportional to temperature. Most temperature sensors have positive coefficient (PTC) (desirable) which means that the sensor output goes up as the temperature goes up.

Some sensors have negative temperature coefficient (NTC) which means that the output goes down as the temperature goes up.

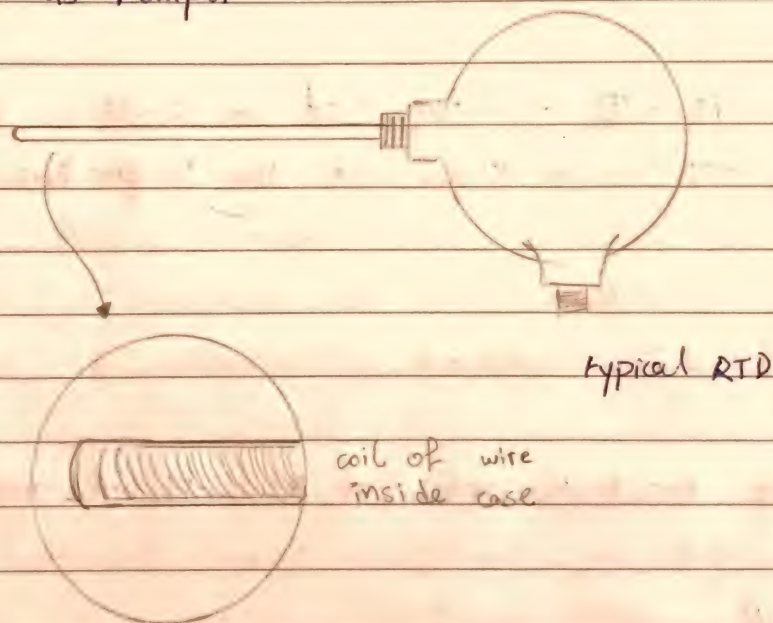RTD : Resistance temperature detectors : is a temperature sensor based on the fact that metals increase in resistance as temper



A wire, such as platinum, is wrapped around a ceramic or glass rod (sometimes the wire coil is supported between two ceramic rods).



RTDs are available in different resistance, a common value being 100Ω . Thus, a 100Ω platinum (Pt 100 RTD) has resistance of 100Ω at 0°C and has sensitivity of $0.39\Omega/^\circ\text{C}$

$$R = R_0 + \alpha \Delta T$$

Some characteristics

Sensitivity: dependent on its kind

Response time: $(0.5 \sim 5)$ sec
الزمن الذي يستغرقه الحساس
للاستجابة لتغير الحرارة

Range: Platinum $(-100^\circ\text{C} \sim 650^\circ\text{C})$

Nicel $(-180^\circ\text{C} \sim 300^\circ\text{C})$

Examples:

A 100Ω Pt RTD is being used in a system. The present resistance reading is 110Ω . Find the temperature.

$$R = 110 - 100 = 10\Omega$$

$$T = \frac{10}{0.39} = 25.6^\circ\text{C}$$

Find the resistance value of 100Ω Pt of 100Ω at 10°C


$$R = 100 + (0.39 * 10)$$

$$R = 103.9\Omega$$



the advantage of RTD is being very accurate and stable. But its disadvantages are low sensitivity, relatively slow response time, and high cost.

RTD linear approximation

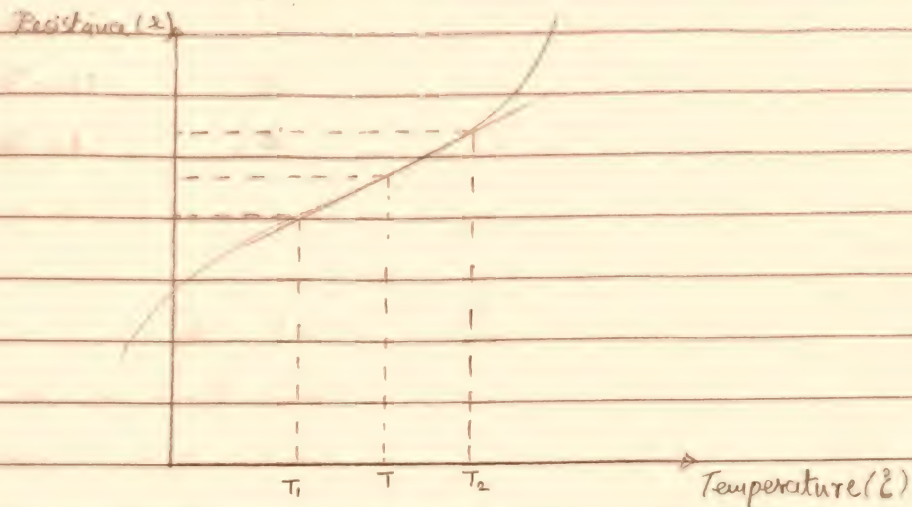

$$R(T) = R(T_0) [1 + \alpha_0 \Delta T] \quad T_1 < T < T_2$$

✓ $R(T_0)$ resistance at temperature T_0

approximation of resistance at temperature T

$$\Delta T = T - T_0$$

α_0 = fractional change in resistance per degree

$$\alpha_0 = \frac{1}{R(T_0)} \cdot \frac{R_2 - R_1}{T_2 - T_1}$$

R_2 = resistance at T_2

R_1 = resistance at T_1



Ex:

Find the linear approximation of resistance versus temperature between 60°F to 90°F

T(°F)

R(Ω)

60

106.0

65

107.6

70

109.1

75

110.2

80

111.1

85

111.7

90

112.2

$$\alpha_0 = \frac{1}{R(T_0)} \cdot \frac{R_2 - R_1}{T_2 - T_1}$$

قيمة المقاومة عند درجة الحرارة T₀
الفرق بين قيمتي المقاومة

$$\alpha_0 = \frac{1}{110.2} \cdot \frac{112.2 - 106.0}{90 - 60} = 1.8753 \text{ m}$$

check your answer

$$R(60^\circ\text{F}) = 107.1$$

$$\text{error} = -1\%$$

$$R(85) = 112.3$$

$$\text{error} = 0.54\%$$

RTD Quadratic approximation

$$R(T) = R(T_0) [1 + \alpha_1 \Delta T + \alpha_2 (\Delta T)^2]$$

where

R(T) = quadratic approximation of the resistance

R(T₀) = resistance at T₀

$$\Delta T = T - T_0$$

α = linear fractional change in resistance with temperature

α₂ = quadratic fractional change in resistance with temperature



Ex:

T (°F)

R (Ω)

Find the quadratic approximation
resistance versus temperature
between 60°F and 90°F

60

106.0

65

107.6

70

109.1

75

110.2

Solution

80

111.1

85

111.7

90

112.2

$$106.0 = 110.2 [1 + \alpha_1 (60 - 75) + \alpha_2 (60 - 75)^2]$$

$$112.2 = 110.2 [1 + \alpha_1 (90 - 75) + \alpha_2 (90 - 75)^2]$$

initially Jan

$$\alpha_1 = 1.8746 \text{ m}$$

$$\alpha_2 = -44.355 \text{ m / (°F)}^2$$

check your answer

$$R(60) = 106.0 \text{ } \Omega$$

$$\text{error} = 0\%$$

$$R(85) = 111.8 \text{ } \Omega$$

$$\text{error} = -0.09\%$$

Note the quadratic approximation provides a much
better approximation of the resistance versus
temperature



Thermocouple Tables

tables give the output voltage over a range of temperature in 5°C increments, the reference temperature is 0°C. The temperature in °C and the output in mV.

in case the measured voltage does not fall exactly on a table value, we use interpolate

$$T_M = T_L + \left[\frac{T_H - T_L}{V_H - V_L} \right] (V_M - V_L)$$

if the temperature does not found

$$V_M = V_L + \left(\frac{V_H - V_L}{T_H - T_L} \right) (T_M - T_L)$$

Ex: A voltage of 23.72 mV is measured with a type K thermocouple at a 0°C reference. Find the temperature of the measurement junction

$V_M = 23.72$ mV does not found in table: so

We use interpolate

$$T_M = 570^\circ\text{C} + \frac{575 - 570}{23.84 - 23.63} (23.72 - 23.63)^\circ\text{C}$$

$$T_M = 572.1^\circ\text{C}$$



Ex: Find the voltage of a type J thermocouple with 0°C reference if the junction temperature -172°C .

$$V_M = -7.27 \text{ mV} + \frac{-7.12 + 7.27}{-770 + 180} (-172 + 175)$$

$$V_M = -7.18 \text{ mV}$$

change of Table reference Termocouple
 it is possible to use tables with TC has a different
 reference temperature by an appropriate shift in
 the table scale.

يعني أنه في حالة كان TC لديه مرجعية أخرى غير الصفر
 فإن قيمة الجهد تساوي

$$\text{قيمة الجهد عند المرجعية الجديدة} = \text{قيمة الجهد عند المرجعية القديمة} - \text{قيمة الجهد عند الصفر الجديد}$$

Example $V_{30}(T) = V_0(T) - V_0(30)$

